

Experiment 3 – Function Generator

Matin
Bazrafshan,
810100093

Mohammad Amin
Yousefi,
810100236

Abstract— This document is a report for experiment 3 of Digital Design Laboratory at ECE department at University of Tehran. The purpose of this experiment is to design a sequence detector and synthesize on an FPGA .

Keywords—DE1 FPGA, Wave Generator, PWM, Oscilloscope, Frequency Selector, Amplitude Selector

I. INTRODUCTION

In this experiment we will design a Wave Generator, First we simulate waves with Verilog in Modelsim, Then using Quartus we implement it on an FPGA and finally we see Waves on an oscilloscope. After that we will see different between using LUT and memory in FPGA.

II. SIMULATION ON VERILOG

A. Wave Generator

This module is the heart of this project. It produces desired functions. Output of this module is an 8-bit digital representing the amplitude of signal. The supported functions, are sine, square, reciprocal, triangle, full-wave and half-wave rectified signals.

 


Fig. 1 Waveforms

```
1 module WaveGenerator (
2     input clock, reset,
3     input [7:0] count,
4     output [7:0] square, triangle, reciprocal, sin, full, half
5 );
6     assign square = (count < 128) ? 0 : 255;
7     assign triangle = (count < 128) ? count << 1 : (255 - count) << 1;
8     assign reciprocal = 255 / (256 - count);
9
10    reg [15:0] snn = 0, cnn = 30000;
11    reg [15:0] sn, cn;
12    always @(posedge clock, posedge reset) begin
13        if (reset) begin
14            snn = 0;
15            cnn = 30000;
16            cn = 0;
17            sn = 30000;
18        end
19        else begin
20            sn = snn + (cnn[15],cnn[15],cnn[15],cnn[15],cnn[15],cnn[15],cnn[15],cnn[15]);
21            cn = cnn - {sn[15],sn[15],sn[15],sn[15],sn[15],sn[15],sn[15],sn[15]};
22            snn = sn;
23            cnn = cn;
24        end
25    end
26
27
28    assign sin = sn[15:8] + 127;
29    assign full = (sin >= 127) ? sin : sin + 2*(127-sin);
30    assign half = (sin >= 127) ? sin : 127;
31 endmodule
32
33
```

Fig. 2 Wave Generator Verilog Code

 


Fig. 3 Waveforms Simulated on Modelsim

B. Digital to Analog conversion using PWM

There are different methods for digital to analog conversion. You can either use an external chip like using an add-on-board card that consists of both ADC and DAC or it can be implemented using Pulse Width Modulation (PWM). The following is a brief description of how PWM works as a DAC.

A PWM signal is a sequence of periods in which the duration of the logic-high (or logic-low) voltage varies according to external conditions, and these variations can be used to transmit information.

The PWM carrier frequency is constant, so the active and inactive state duration increase or decrease vice versa. The duty cycle of the PWM signal is equal to:

$$duty\ cycle = \frac{T_{on}}{T_{on} + T_{off}}$$

```

1 module PWM (
2     input [7:0] signal_in,
3     input clock, reset,
4     output reg signal_out
5 );
6     reg [7:0] counter = 0;
7     always@(posedge clock, posedge reset) begin
8
9         if (reset)
10            counter = 0;
11
12        else begin
13
14            if (counter < signal_in)
15                signal_out <= 1;
16            else
17                signal_out <= 0;
18
19            counter = counter + 1;
20        end
21    end
22 end
23 endmodule

```

Fig. 4 PWM Verilog Code

C. Frequency Selector

In order to set the frequency of the output signal a frequency selector is required. The frequency selector consists of a counter that divides a high source input signal to the desired value.

We use a 9-bit counter with 3 most-left bits can be loaded and 6 bits are fixed.

```

1 module FrequencySelector (
2     input clock, reset, load,
3     input [3:0] par_in,
4     output reg low_freq_clock
5 );
6
7     reg [4:0] fixed = 0;
8     reg [8:0] count;
9     wire carry;
10    initial begin
11        low_freq_clock = 0;
12        count = {par_in, fixed};
13    end
14    always @(posedge clock, posedge reset) begin
15
16        if(reset)
17            count = {par_in, fixed};
18        else if((~load) || carry)
19            count = {par_in, fixed};
20        else
21            count = count + 1;
22    end
23 end
24
25 assign carry = &{count};
26
27 always @(posedge carry) begin
28     low_freq_clock = ~low_freq_clock;
29 end
30
31 endmodule

```

Fig. 5 9-bit counter with 6 fixed bits and 3 loadable bits

D. Amplitude Selector

One option in function generator is the amplitude of generated wave. The task of this module is to scale down the amplitude of the waveforms. This can be done by dividing the output amplitude by a number

SW[6:5]	Amplitude
2'b00	1
2'b01	2
2'b10	4
2'b11	8

Fig. 6 Divide Select in Amplitude Selector

```

1 module AmpSelector (
2     input [7:0] wave_in,
3     input [1:0] select,
4     output reg [7:0] wave_out
5 );
6
7 always begin
8     case (select)
9         0: wave_out = wave_in;
10        1: wave_out = {1'b0, wave_in[7:1]};
11        2: wave_out = {2'b0, wave_in[7:2]};
12        3: wave_out = {3'b0, wave_in[7:3]};
13        default: wave_out = wave_in;
14    endcase
15 end
16
17 endmodule

```

Fig. 7 Amplitude Selector Verilog Code

III. SYNTHESIS

After designing every module, we get an instantiate in Quartus, and then we connect them properly.

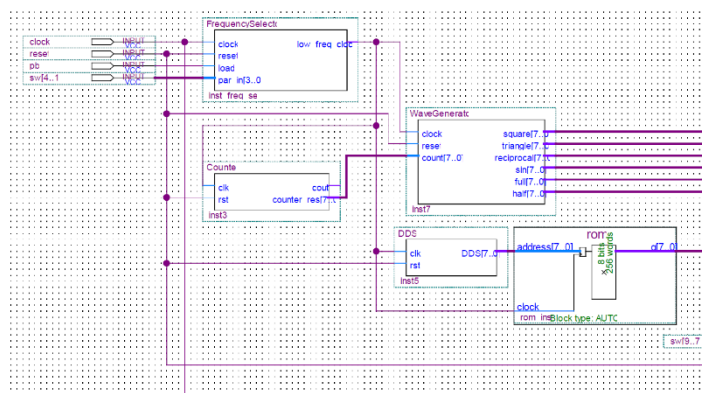


Fig. 8 Block Diagram Part I

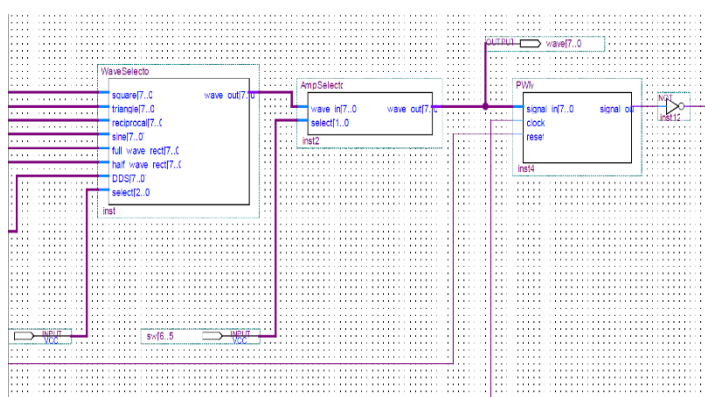


Fig. 9 Block Diagram Part II (Right Hand Side of Part I)

IV. WAVES ON OSCILLOSCOPE

The output will be given to a Low pass filter (An RC circuit) and then connected to a oscilloscope.

Take note that the output is connected to a NOT, so it is shown in reverse.



Fig.10 Reciprocal Wave

 


Fig.11 Triangle Wave


 


Fig.12 Sine Wave

 

 


Fig.19 Sine Wave with Amp 1/4

 


Fig.20 Sine Wave with Amp 1/8

V. DDS AND ROM

Most modern function generators use Direct Digital Synthesis (DDS) for generating their output waveforms. DDS is used for generating arbitrary phase tunable output from a single fixed-frequency reference clock (like an oscillator). The output of DDS module is a quantized version of the output files (usually a sinusoid). The period of this signal is controlled by a Phase control value. To generate the DDS signal, you should use a 1-port ROM memory to store the value of a sine wave for several clock cycles.

In FPGA if we get a ROM instantiate from synthesizer (like Quartus) it will use a memory instruction as a ROM but if we want to write a ROM module manually we can use an LUT or a memory instruction as a ROM, using memory is more efficient so we must declare in our code that we want to use a memory instead of LUT because LUT is chosen default.

```

1 module ROM (
2     input clock,
3     input [7:0] address,
4     output reg [7:0] out
5 );
6 // " (* romstyle = "M9K" *) " is written to use memory instead of LUT
7 (* romstyle = "M9K" *) (* ram_init_file = "sine.mif" *) reg [7:0] mem [7:0];
8
9 always @(posedge clock) begin
10     out = mem[address];
11 end
12
13 endmodule

```

Fig.21 ROM Verilog Code

```

1 module DDS (
2     input clk, rst,
3     output [7:0] DDS
4 );
5 reg [7:0] address = 0;
6 always @(posedge clk, posedge rst) begin
7     if(rst)
8         address = 8'b0;
9     else begin
10         address = address + 1;
11     end
12 end
13
14 assign DDS = address;
15 endmodule

```

Fig.22 DDS Verilog Code

 


Fig.23 Sine Wave Using DDS

 


Fig.24 Using a LUT as a ROM in FPGA

 


Fig.25 Using a Memory as a ROM in FPGA

VI. EFFECT OF CAPACITOR ON SMOOTHING

As we increase capacitance of RC circuit, the sampling will be better and the output becomes more smoother.

 


Fig.26 Sine Wave With 10 nF Capacitor

 


Fig.27 Sine Wave With 200 nF Capacitor